

Yashwantrao Chavan College of Science, Karad

Question Bank

Linear and Digital integrated circuits (Electronics Paper No.- IV)

MCQ

1. Flip-flop is a circuit
 - a) Astable
 - b) Monostable
 - c) Bistable**
 - d) Schmitt trigger
2. In a D Flip-flop.....input is called synchronous input of the flip-flop.
 - a) reset
 - b) preset
 - c) clear
 - d) D**
3. Shift register consist of number of
 - a) transistor
 - b) ICs
 - c) flip-flops**
 - d) Latches
4. The IC 7495 is a
 - a) counter
 - b) up/down counter**
 - c) decade counter
 - d) shift register
5. The IC.....can be used for synchronous decade counter.
 - a) 7492
 - b) 7493
 - c) 7490**
 - d) 7491
6. R-2R ladder network is used for.....conversion.
 - a) analog to digital
 - b) digital to analog**
 - c) digital to parallel
 - d) all of these
7. Successive approximation method is used for.....
 - a) ADC**
 - b) DAC
 - c) AAC
 - d) DDC
8. An ideal Op-amp hasinput impedance.
 - a) 0Ω
 - b) 75Ω
 - c) $2M\Omega$
 - d) infinite Ω**
9. For an idea Op-amp, the slew rate is

- 34) In dual slope conversion method, conversion time is
(a) very small (b) large (c) zero (d) very large
- 35) In an integrator, the feedback element is a.....
(a) resistor (b) **capacitor**
(c) diode (d) zener diode
- 36) Zero-level detector is one application of a
(a) diode (b) differentiator
(c) **comparator** (d) integrator
- 37) The Wien Bridge oscillator is useful
(a) At high frequencies (b) **At low frequencies**
(c) At small input signal (d) In LC circuit
- 38) An ideal Op-Amp has.....output impedance.
(a) **0 Ω** (b) $2M\ Ω$ (c) $75\ Ω$ (d) infinite $Ω$
- 39) Op-Amp is basically.....
(a) DC amplifier (b) RC coupled amplifier
(c) **differential amplifier** (d) none of these
- 40) The parameter which decides the speed of Op-Amp is....
(a) SVRR (b) CMRR (c) **slew rate** (d) UGB
- 41) An astable multivibrator has stable state.
(a) one (b) two (c) **no** (d) one quasi
- 42) In IC 555 timer, the pin number 7 stands for.....
(a) threshold (b) reset (c) trigger (d) **discharge**

Q2) Attempt any two of the following: (10 marks each)

[20]

- a) Explain Op-Amp as inverting and non- inverting amplifier.
- b) Explain the functional block diagram of IC 555.
- c) With proper circuit diagram, explain in detail R-2R ladder method of DAC.
- d) Explain the working of RS flip- flop using transistor with truth table.
- e) Describe the working of JK flip-flop with logic diagram and truth table
- f) Explain the brief 4- bit left shift and right shift register with proper diagram.

Q3) Attempt any four of the following: (5 marks each)

[20]

- a) Explain the working of RS flip- flop using NOR gate.
- b) Explain the working of D flip- flop and state its advantages.

- c) Draw the logic diagram of SIPO shift register and explain it.
- d) Explain 4 –bit ring counter.
- e) Explain the up/ down counter.
- f) Explain the frequency response of Op- Amp.
- g) What is an Op-Amp? Give its schematic symbol and its equivalent circuit.
- h) 7. Define the following parameters:
 - (a) Input offset current, (b) Input offset voltage, (c) Input bias current.
- i) List the features of ADC 0804.
- j) Explain in short successive approximation method of ADC.
- k) Define the terms:
 - (a) Accuracy, (b) Resolution, (c) Settling time.
- l) Explain the working of D flip- flop and state its advantages.
- m) Explain 4 –bit asynchronous binary counter.
- n) Explain the JK flip flop.
- o) Explain preset and clear facilities in D flip-flop, draw its logic diagram.
- p) Explain the frequency response of Op- Amp.
- q) Explain the working of RS flip- flop using NAND gate.
- r) What is meant by shift register? Give types of shift register.
- s) Draw the logic diagram of PIPO shift register and explain it